


Microwave Project Methodology

Step 1: Tapered line selection

Choosing Blackman-Harris because it offers excellent side lobe suppression, which significantly reduces spectral leakage.

Step 2: Simulation

 In this step we use Python, on Google Colab, to visualize the taper line behavior through characteristic Impedance versus distance from source $[z/L]$ from 50Ω to 100Ω plot and the Reflection Coefficient in decibel versus βL plot. We also use Python to compute the impedance of each section in this step, we number of sections equal 10. The plots are shown below:



The computed impedance for each section is saved as table, as shown below:

	0
0	50
1	50.1062102
2	51.11348314
3	55.0701908
4	64.19909417
5	77.88271882
6	90.79322092
7	97.82154714
8	99.78802987
9	100

Then we import it to Google Sheet and modify it to be ready for Sonnet file format:

TLIN	1	2	Z=	50	E=	36.00	F=	4.00	TLIN 1 2 Z=50.0 E=36.0 F=4.0
TLIN	2	3	Z=	50.1062102	E=	36.00	F=	4.00	TLIN 2 3 Z=50.1 E=36.0 F=4.0
TLIN	3	4	Z=	51.11348314	E=	36.00	F=	4.00	TLIN 3 4 Z=51.1 E=36.0 F=4.0
TLIN	4	5	Z=	55.0701908	E=	36.00	F=	4.00	TLIN 4 5 Z=55.1 E=36.0 F=4.0
TLIN	5	6	Z=	64.19909417	E=	36.00	F=	4.00	TLIN 5 6 Z=64.2 E=36.0 F=4.0
TLIN	6	7	Z=	77.88271882	E=	36.00	F=	4.00	TLIN 6 7 Z=77.9 E=36.0 F=4.0
TLIN	7	8	Z=	90.79322092	E=	36.00	F=	4.00	TLIN 7 8 Z=90.8 E=36.0 F=4.0
TLIN	8	9	Z=	97.82154714	E=	36.00	F=	4.00	TLIN 8 9 Z=97.8 E=36.0 F=4.0
TLIN	9	10	Z=	99.78802987	E=	36.00	F=	4.00	TLIN 9 10 Z=99.8 E=36.0 F=4.0

Step 3: netlist simulation inside sonnet


Since both sides of the tapered line are symmetry we simply extend the table as shown below before using the rightmost column for modifying the Sonnet netlist file.

TLIN	1	2	Z=	50	E=	36.00	F=	4.00	TLIN 1 2 Z=50.0 E=36.0 F=4.0
TLIN	2	3	Z=	50.1062102	E=	36.00	F=	4.00	TLIN 2 3 Z=50.1 E=36.0 F=4.0
TLIN	3	4	Z=	51.11348314	E=	36.00	F=	4.00	TLIN 3 4 Z=51.1 E=36.0 F=4.0
TLIN	4	5	Z=	55.0701908	E=	36.00	F=	4.00	TLIN 4 5 Z=55.1 E=36.0 F=4.0
TLIN	5	6	Z=	64.19909417	E=	36.00	F=	4.00	TLIN 5 6 Z=64.2 E=36.0 F=4.0
TLIN	6	7	Z=	77.88271882	E=	36.00	F=	4.00	TLIN 6 7 Z=77.9 E=36.0 F=4.0
TLIN	7	8	Z=	90.79322092	E=	36.00	F=	4.00	TLIN 7 8 Z=90.8 E=36.0 F=4.0
TLIN	8	9	Z=	97.82154714	E=	36.00	F=	4.00	TLIN 8 9 Z=97.8 E=36.0 F=4.0
TLIN	9	10	Z=	99.78802987	E=	36.00	F=	4.00	TLIN 9 10 Z=99.8 E=36.0 F=4.0
TLIN	10	11	Z=	100	E=	36.00	F=	4.00	TLIN 10 11 Z=100.0 E=36.0 F=4.0
TLIN	11	12	Z=	100	E=	36.00	F=	4.00	TLIN 11 12 Z=100.0 E=36.0 F=4.0
TLIN	12	13	Z=	99.78802987	E=	36.00	F=	4.00	TLIN 12 13 Z=99.8 E=36.0 F=4.0
TLIN	13	14	Z=	97.82154714	E=	36.00	F=	4.00	TLIN 13 14 Z=97.8 E=36.0 F=4.0
TLIN	14	15	Z=	90.79322092	E=	36.00	F=	4.00	TLIN 14 15 Z=90.8 E=36.0 F=4.0
TLIN	15	16	Z=	77.88271882	E=	36.00	F=	4.00	TLIN 15 16 Z=77.9 E=36.0 F=4.0
TLIN	16	17	Z=	64.19909417	E=	36.00	F=	4.00	TLIN 16 17 Z=64.2 E=36.0 F=4.0
TLIN	17	18	Z=	55.0701908	E=	36.00	F=	4.00	TLIN 17 18 Z=55.1 E=36.0 F=4.0
TLIN	18	19	Z=	51.11348314	E=	36.00	F=	4.00	TLIN 18 19 Z=51.1 E=36.0 F=4.0
TLIN	19	20	Z=	50.1062102	E=	36.00	F=	4.00	TLIN 19 20 Z=50.1 E=36.0 F=4.0
TLIN	20	21	Z=	50	E=	36.00	F=	4.00	TLIN 20 21 Z=50.0 E=36.0 F=4.0

Now, we have the netlist file. The units are left as default, our netlist has 2 ports, and both ports have 50 Ohms resistance. Then we sweep from 0 to 8 GHz frequency. Here is the netlist:

Element	Nodes	Description
Net	1 21	Main Network
TLIN	1 2	Z=50.0 E=36.0 F=4.0
TLIN	2 3	Z=50.1 E=36.0 F=4.0
TLIN	3 4	Z=51.1 E=36.0 F=4.0
TLIN	4 5	Z=55.1 E=36.0 F=4.0
TLIN	5 6	Z=64.2 E=36.0 F=4.0
TLIN	6 7	Z=77.9 E=36.0 F=4.0
TLIN	7 8	Z=90.8 E=36.0 F=4.0
TLIN	8 9	Z=97.8 E=36.0 F=4.0
TLIN	9 10	Z=99.8 E=36.0 F=4.0
TLIN	10 11	Z=100.0 E=36.0 F=4.0
TLIN	11 12	Z=100.0 E=36.0 F=4.0
TLIN	12 13	Z=99.8 E=36.0 F=4.0
TLIN	13 14	Z=97.8 E=36.0 F=4.0
TLIN	14 15	Z=90.8 E=36.0 F=4.0
TLIN	15 16	Z=77.9 E=36.0 F=4.0
TLIN	16 17	Z=64.2 E=36.0 F=4.0
TLIN	17 18	Z=55.1 E=36.0 F=4.0
TLIN	18 19	Z=51.1 E=36.0 F=4.0
TLIN	19 20	Z=50.1 E=36.0 F=4.0
TLIN	20 21	Z=50.0 E=36.0 F=4.0

Sweeps from 0 to 8 GHz:

 

Step 4: geometry simulation inside sonnet

After confirming the expected result from netlist, we now use TXLINE 2003 to convert impedance, frequency and electrical length to Length and Width of the copper piece on the PCB.

Example of using TXLINE 2003 to convert the first tapered line section in netlist to length and width:

The screenshot shows the TXLINE 2003 - Microstrip software window. The 'Microstrip' tab is selected. The 'Material Parameters' section includes a dropdown for 'Dielectric' set to 'GaAs', a dropdown for 'Conductor' set to 'Copper', a text input for 'Dielectric Constant' at 4.4, a text input for 'Conductivity' at 5.88E+07 S/m, and a text input for 'Loss Tangent' at 0.015. An AWR logo is present. To the right is a diagram of a microstrip line on a substrate with parameters W, H, ϵ_r , and T. The 'Electrical Characteristics' section on the left contains inputs for Impedance (50 Ohms), Frequency (4 GHz), Electrical Length (36 deg), Phase Constant (8869.05 deg/m), Effective Diel. Const. (3.40934), and Loss (9.78715 dB/m). The 'Physical Characteristic' section on the right contains outputs for Physical Length (L) (4.05906 mm), Width (W) (3.04717 mm), Height (H) (1.6 mm), and Thickness (T) (0.03156 mm). Blue arrows indicate the conversion from electrical to physical characteristics.

Material Parameters		
Dielectric	GaAs	Conductor
Dielectric Constant	4.4	Conductivity
Loss Tangent	0.015	S/m

Electrical Characteristics		
Impedance	50	Ohms
Frequency	4	GHz
Electrical Length	36	deg
Phase Constant	8869.05	deg/m
Effective Diel. Const.	3.40934	
Loss	9.78715	dB/m


Physical Characteristic		
Physical Length (L)	4.05906	mm
Width (W)	3.04717	mm
Height (H)	1.6	mm
Thickness (T)	0.03156	mm

After converting every tapered line section in netlist to length and width, we need to reduce floating points of the dimensions to match Sonnet's resolution.


Then we get this as dimensions for each copper piece which represent each section of the tapered line:

section	Length, X	width Y,	unit mm
1	4.06	3.05	
2	4.06	3.04	
3	4.07	2.94	
4	4.09	2.58	
5	4.15	1.93	
6	4.22	1.28	
7	4.27	0.88	
8	4.30	0.72	
9	4.31	0.68	
10	4.31	0.67	
11	4.31	0.67	
12	4.31	0.68	
13	4.30	0.72	
14	4.27	0.88	
15	4.22	1.28	
16	4.15	1.93	
17	4.09	2.58	
18	4.07	2.94	
19	4.06	3.04	
20	4.06	3.05	

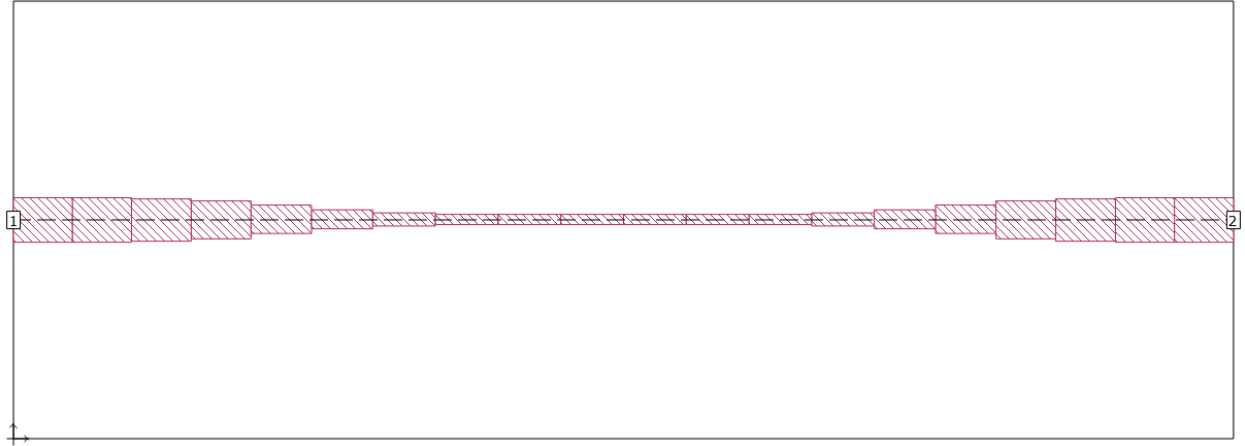
Now we can draw the taper line in the Sonnet geometry file. After we carefully drew the first half (10 sections) of the tapered line, we can copy and flip them, then connect 2 halves together to form the complete tapered line, and lastly we attach 1 port on each side.



 Sweeps from 0 to 8 GHz with step size 0.2 GHz:



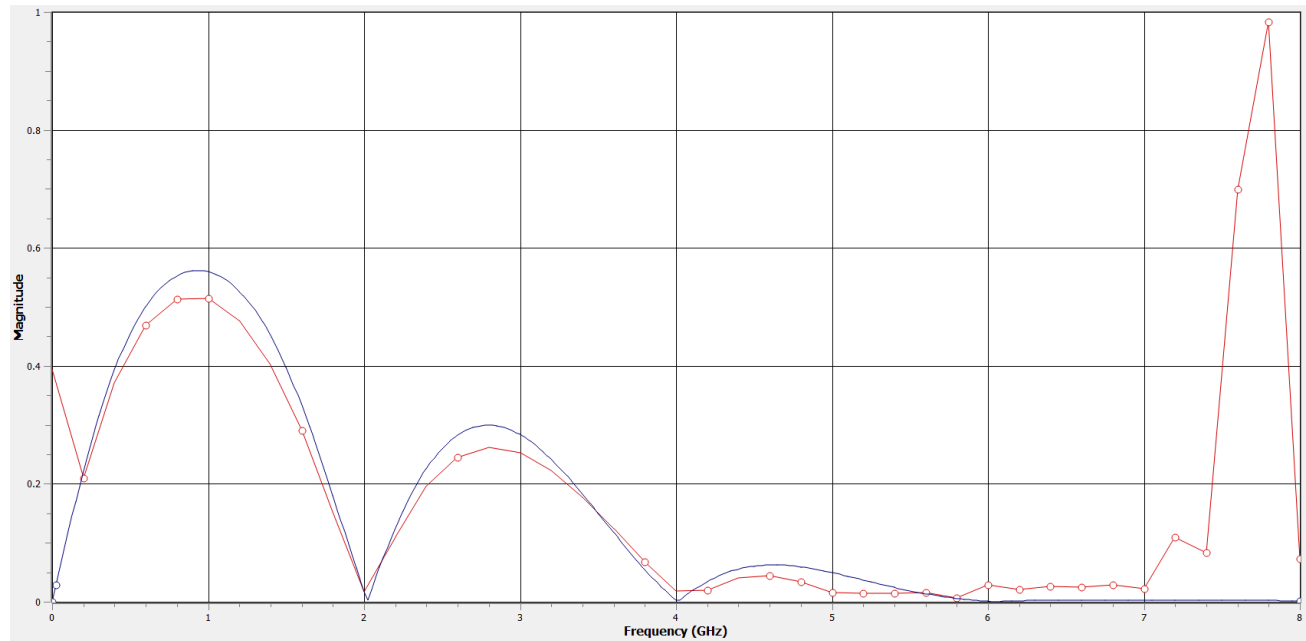
We can see how the geometry sweep (red line) and netlist sweep (blue line) closely resemble each other at 0 to 7 GHz frequency, which is acceptable.



Step 6: Fabrication

After getting acceptable results, we can export geometry file as .DXF file format, we can then import it to EasyEDA, we import .DXF file to the top layer and fill the shape, then erase the perimeter, connect the ports with the same specifications as the actual one, then we place track of the copper from the first and last section to the connector.

 After we confirmed the work is ready, we combine our work with Chayakorn to create the PCB with 2 tapered lines for the efficient fabrication and costing.



After this, we simply export it to be fabricated by JLCPCB.


Link for EasyEDA projects:

Our group's work: <https://oshwlab.com/ratchaphon.su/microvave>

Step 7: Testing

After receiving the fabricated PCB, we connect to ports, i.e. solder the connectors onto them, and test for actual performance.

 The actual performance is plotted in orange, even though it is far from ideal result, it does show some resemblance at lower frequency.



The files used in this report can be accessed through this github repository:

<https://github.com/ayayaay/Microwave-Final-Project-2025.git>

The Google Colab Notebook used for calculating impedance of each Tapered Line section:

<https://colab.research.google.com/drive/1QCjdPgscnVdrFDpWlq8xoF2qkLSR5d8q?usp=sharing>